

-
-
-

`/usr/share/doc/alliance-doc-5.0/tutorial/synthesis/src`


-
-


-

-


-
-

-
-
-
-
-

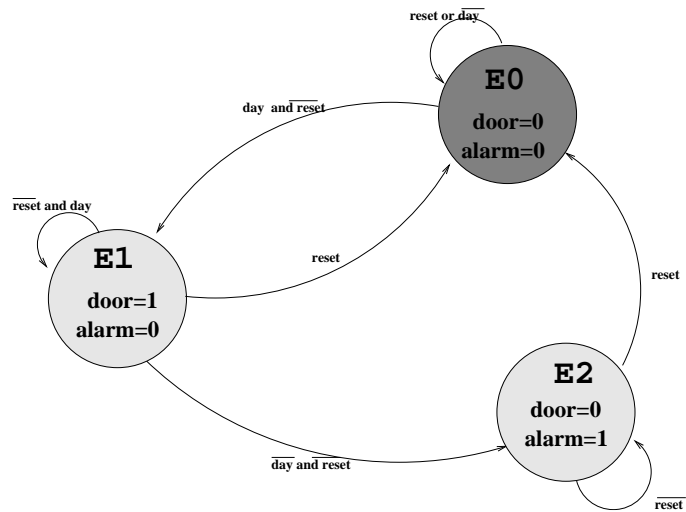


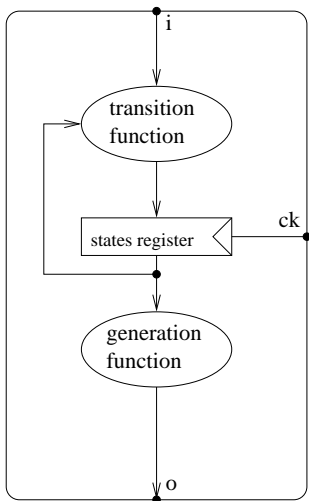

Moore Automat

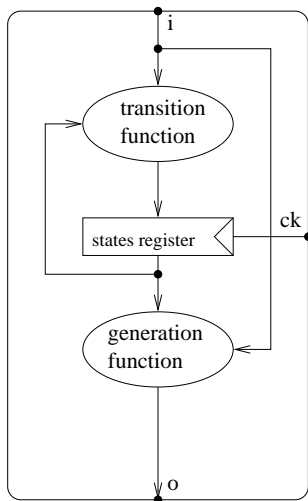

Mealy Automat

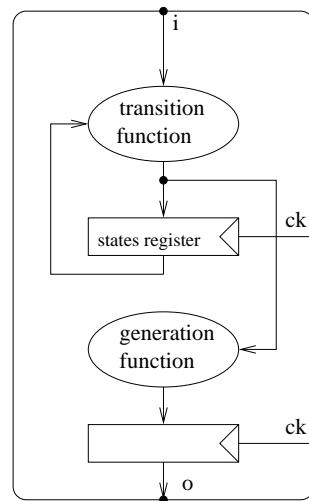


*Moore Automat optimized
on propagation time of o*

```

entity circuit is
    port (
        ck, i, reset, vdd, vss : in bit;
        o : out bit
    );
end circuit;
architecture MOORE of circuit is
    type ETAT _TYPE is (E0, E1, E2, E3);
    signal EF, EP : ETAT _TYPE;
- - pragma CURRENT _STATE EP
- - pragma NEXT _STATE EF
- - pragma CLOCK CK
    begin
        process (EP, i, reset)
        begin
            if (reset='1') then
                EF<=E0;
            else
                case EP is
                    when E0 =
                        if (i='1') then
                            EF <= E1;
                        else
                            EF <= E0;
                        end if;
                    when E1 =
                        if (i='1') then
                            EF <= E2;
                        else
                            EF <= E0;
                        end if;
                    when E2 =
                        if (i='1') then
                            EF <= E3;
                        else
                            EF <= E0;
                        end if;
                    when E3 =
                        if (i='1') then
                            EF <= E3;
                        else
                            EF <= E0;
                        end if;
                    when others = assert ('1')
                        report "etat illegal";
                end case;
            end if;
            case EP is
                when E0 =
                    o <= '0' ;
                when E1 =
                    o <= '0' ;
                when E2 =
                    o <= '0' ;
                when E3 =
                    o <= '1' ;
                when others = assert ('1')
                    report "etat illegal";
            end case;
        end process;
        process(ck)
        begin
            if (ck='1' and not ck'stable) then
                EP <= EF;
            end if;
        end process;
    end MOORE;
end


```

 

-
-

```
> syf -CEV -a <fsm_source>
```

- -
-

 

•

•

•

•

•


•

•

•

•

-
-
-
-
-

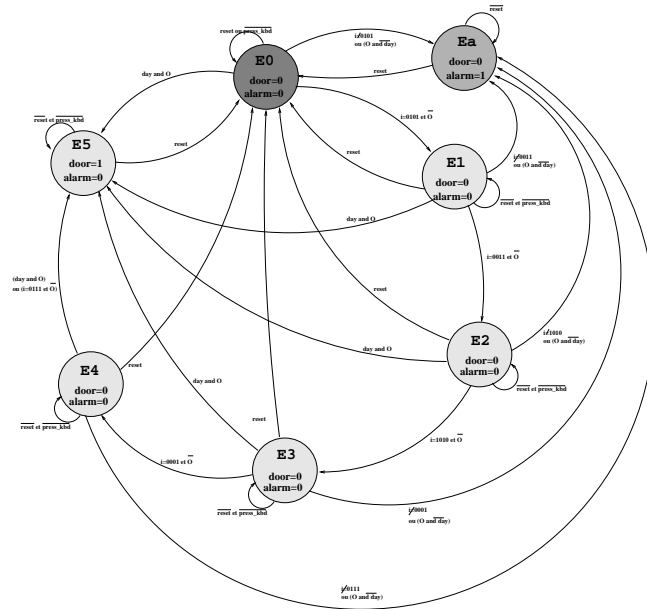


-
-
-

```
> syf -CEV -a <fsm_source>
```

-
-

-
-

 T: intrinsic time
 R: equivalent resistor of AND
 C: equivalent capacity of NOR



-
- -

```
> boog <vbe_source>
```

-
-

-

```
>xsch -I vst -l <vst_source>
```

-
-

-

```
>boom -V <vbe_source> <vbe_destination>
```

-
-
-

-

```
>loon <vst_source> <vst_destination> <lax_param>
```

-

-

-

-

```
>flatbeh <vst_source> <vbe_dest>
```

```
>proof -d <vbe_origin> <vbe_dest>
```

-

```
>scapin -VRB <vst_source> <path_file> <vst_dest>
```

```
BEGIN_PATH_REG
```

```
cs_0
```

```
cs_1
```

```
cs_2
```

```
END_PATH_REG
```

```
BEGIN_CONNECTOR
```

```
SCAN_IN      scin
```


```
SCAN_OUT     scout
```

```
SCAN_TEST    test
```


```
END_CONNECTOR
```

●


-
-
-
-
-
-
-

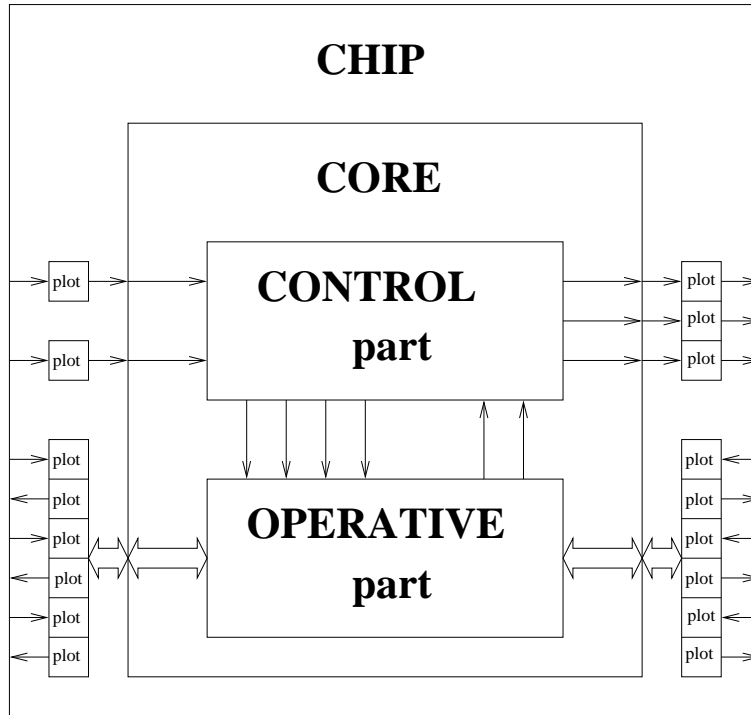

-
-

 

•
•
•
•
•
•
•
•
•
•

 

```
#include <genlib.h>
main()
{
    GENLIB_DEF_LOFIG("circuit");

    /* Connectors declaration */
    GENLIB_LOCON("a", IN, "a1");
    GENLIB_LOCON("b", IN, "b1");
    GENLIB_LOCON("c", IN, "c1");
    GENLIB_LOCON("d", IN, "d1");
    GENLIB_LOCON("e", IN, "e1");
    GENLIB_LOCON("s", OUT, "s1");

    GENLIB_LOCON("vdd", IN, "vdd");
    GENLIB_LOCON("vss", IN, "vss");

    /* Combinatorial gates instanciation */
    GENLIB_LOINS("na2_x1", "nand2", "a1", "c1", "f1", "vdd", "vss", 0);
    GENLIB_LOINS("no2_x1", "nor2", "b1", "e1", "g1", "vdd", "vss", 0);
    GENLIB_LOINS("o2_x2", "or2", "d1", "f1", "h1", "vdd", "vss", 0);
    GENLIB_LOINS("inv_x1", "inv", "g1", "i1", "vdd", "vss", 0);
    GENLIB_LOINS("a2_x2", "and2", "h1", "i1", "s1", "vdd", "vss", 0);

    /* Save of the figure */
    GENLIB_SAVE_LOFIG();
    exit(0);
}
```

```
> genlib circuit
```



```
amd2901_ctl C  
amd2901_dpt C
```

```
> asimut amd2901_chip pattern result
```

```
> genlib amd2901_ctl
```

```
> asimut -zerodelay amd2901_chip vecteurs result
```
  
```
> asimut amd2901_chip pattern result
```



```

#include <genlib.h>
main()
{
    GENLIB_DEF_LOFIG("data_path");

    /* connectors declaration */
    GENLIB_LOCON("a[3:0]", IN, "a[3:0]");
    GENLIB_LOCON("b[3:0]", IN, "b[3:0]");
    GENLIB_LOCON("c[3:0]", IN, "c[3:0]");
    GENLIB_LOCON("v", IN, "v");
    GENLIB_LOCON("cout", OUT, "ct");
    GENLIB_LOCON("s[3:0]", OUT, "s[3:0]");
    GENLIB_LOCON("cmd", IN, "cmd");
    GENLIB_LOCON("vdd", IN, "vdd");
    GENLIB_LOCON("vss", IN, "vss");

    /* operators creation */
    GENLIB_MACRO(GEN_NAND2, "model_nand2_4bits", F_PLACE, 4, 1);
    GENLIB_MACRO(GEN_OR2, "model_or2_4bits", F_PLACE, 4);
    GENLIB_MACRO(GEN_ADSB2F, "model_add2_4bits", F_PLACE, 4);

    /* operators Instanciation */
    GENLIB_LOINS("model_nand2_4bits", "model_nand2_4bits",
        "v", "v", "v", "v",
        "a[3:0]",
        "d_aux[3:0]",
        vdd, vss, NULL);
    GENLIB_LOINS("model_or2_4bits", "model_or2_4bits",
        "d_aux[3:0]",
        "b[3:0]",
        "e_aux[3:0]",
        vdd, vss, NULL);
    GENLIB_LOINS("model_add2_4bits", "model_add2_4bits",
        "cmd",
        "cout",
        "ovr",
        "e_aux[3:0]",
        "c[3:0]",
        "s[3:0]",
        vdd, vss, NULL);


    /* Save of figure */
    GENLIB_SAVE_LOFIG();
    exit(0);
}

```

```
> genlib data_path
```

```
> genlib amd2901_dpt
```
 
```
> asimut -zerodelay amd2901_chip pattern result
```



```
target1 : dependence1 dependence2 ....
#Rq: each command must be preceded by a tabulation
command_X
command_Y
.
.
.
```

```
#example of rule for the synthesis
%.vst : %.vbe
    boog $*
```

```
#variables definitions
MY_COPY  = cp -r
MY_NUM   = 42
MY_STRING="hello"
```


```
#use a variable in a rule

copy:
    ${MY_COPY} digicode.vbe tmp/
```

•
•
•
•


• ^
•
•


Decoding of the multiplexers R and S.

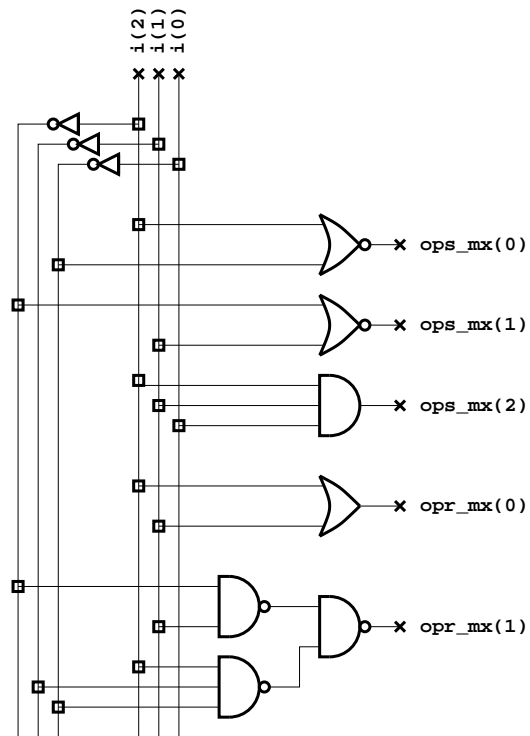


$ops_mx(0) = (\text{not } i(2)) \text{ and } i(0)$
 $ops_mx(1) = i(2) \text{ and } (\text{not } i(1))$
 $ops_mx(2) = i(2) \text{ and } i(1) \text{ and } i(0)$


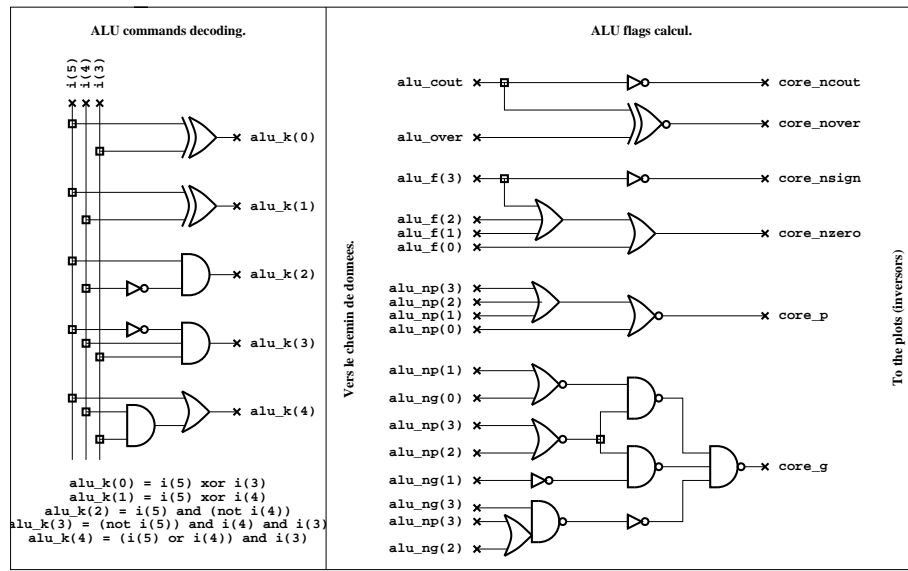
$opr_mx(0) = i(2) \text{ or } i(1)$
 $opr_mx(1) = ((\text{not } i(2) \text{ and } i(1)) \text{ or } (i(2) \text{ and } (\text{not } i(1)) \text{ and } (\text{not } i(0))))$



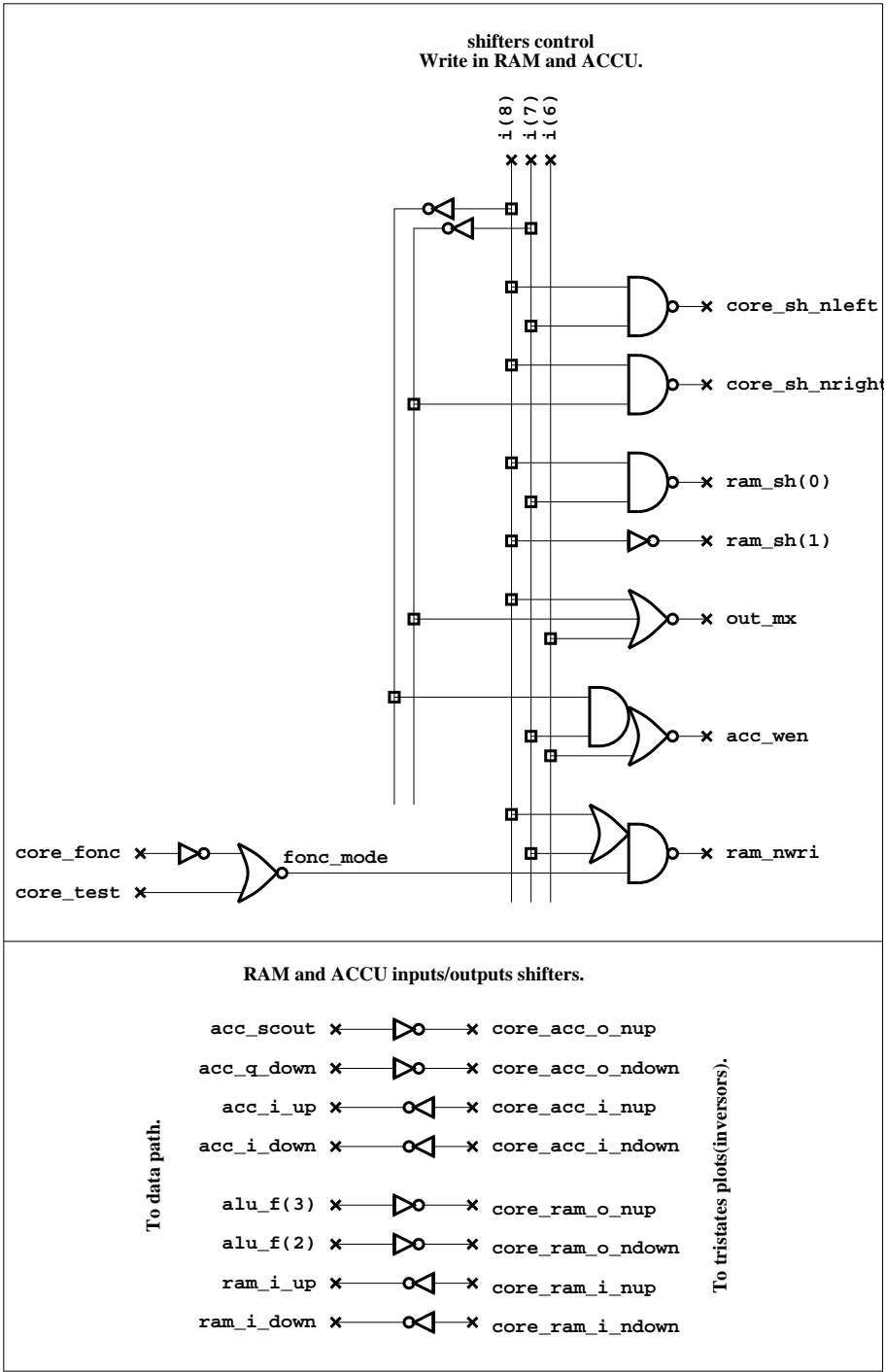


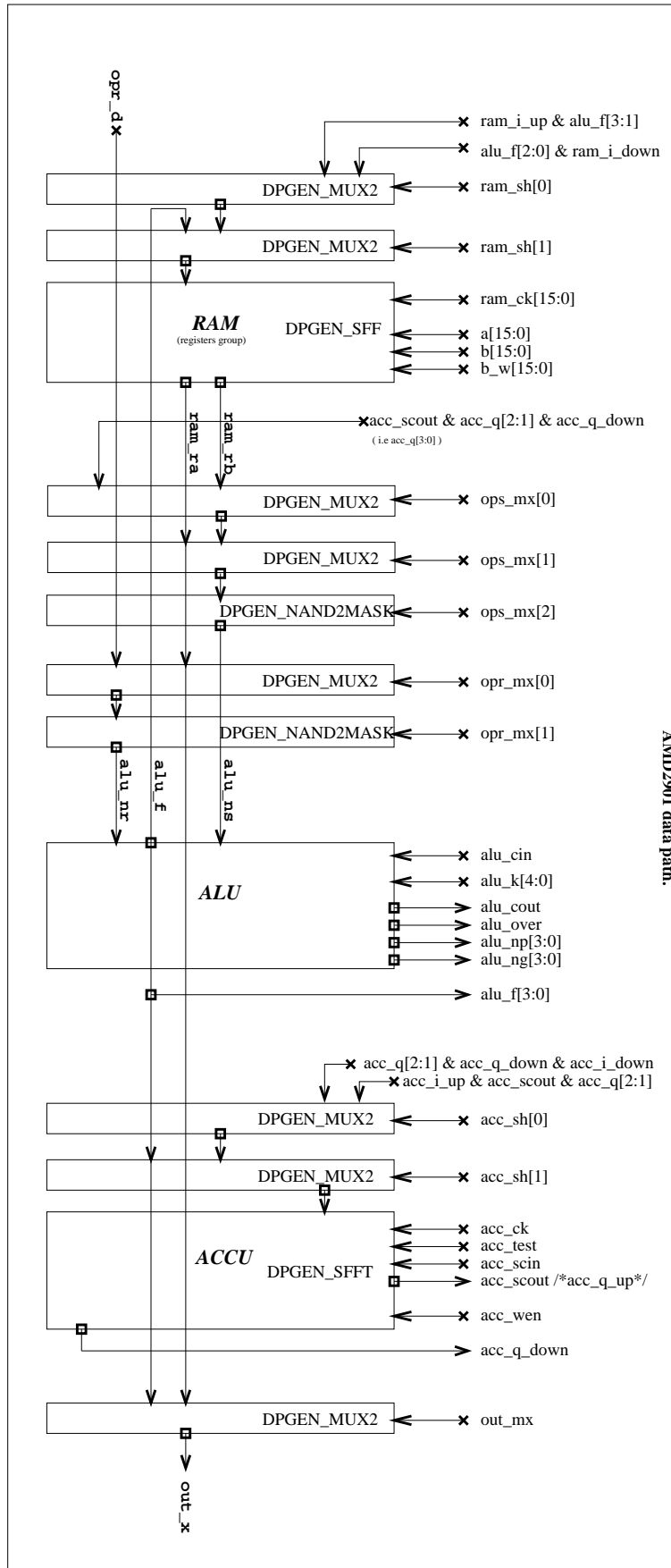

AMD2901 data path.

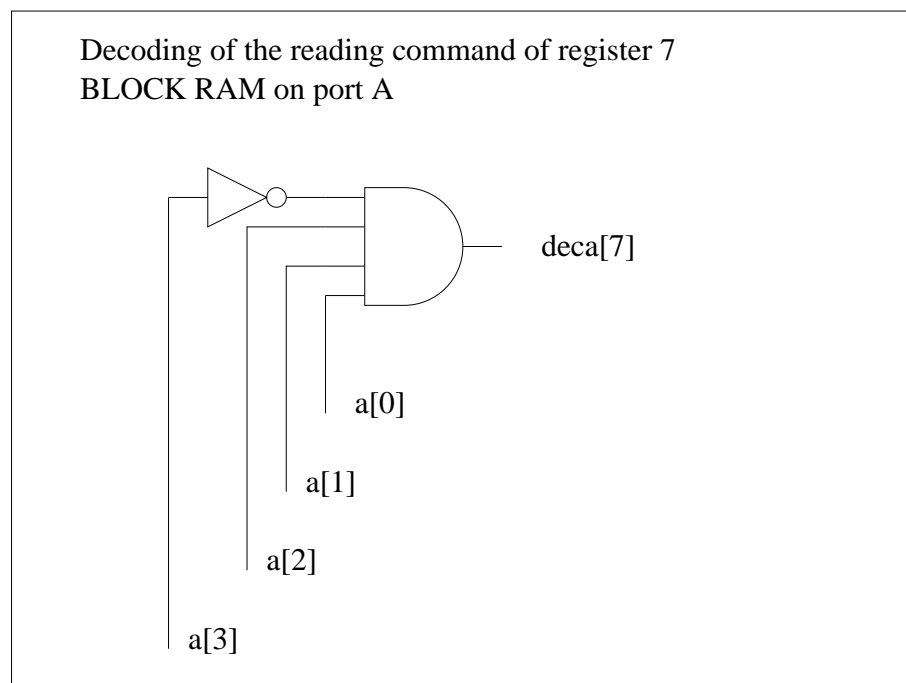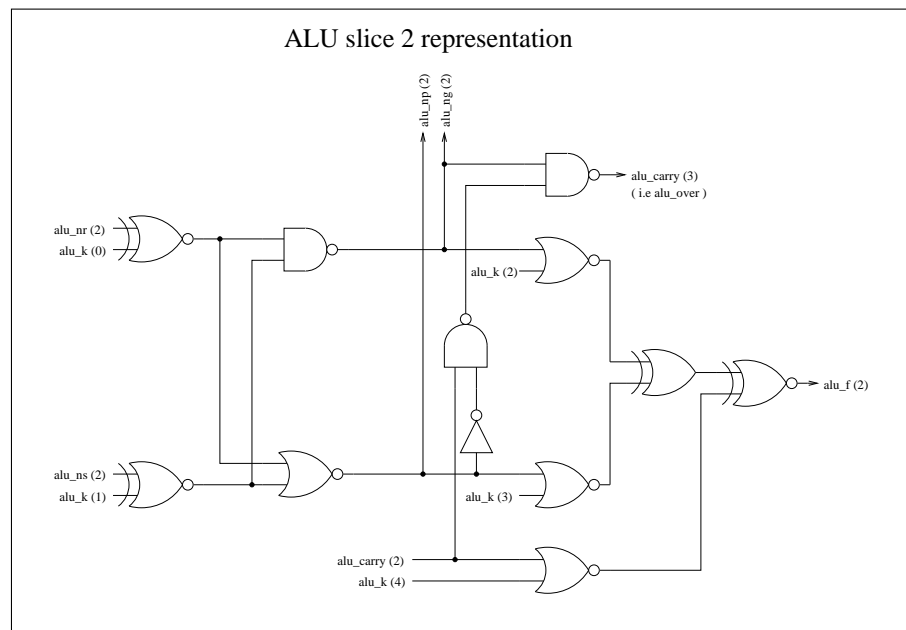

 write decoding command in register 7 of BLOCK RAM



Slice 7 of BLOCK RAM

